

IMAGES USED TO AID IN DESIGN FLOW FOR MINI SRC

PHASE 1:

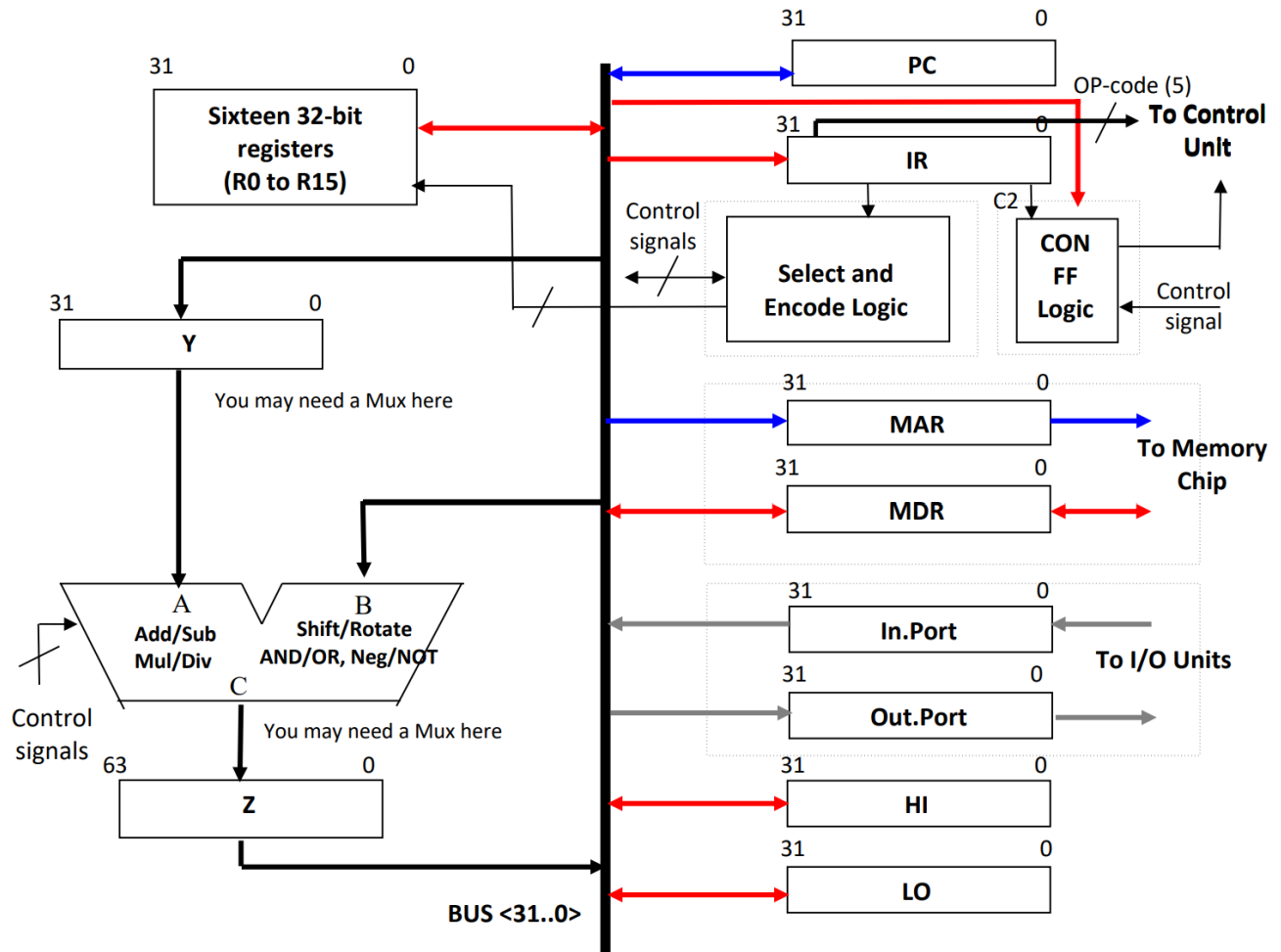


Figure 1: Simplified datapath

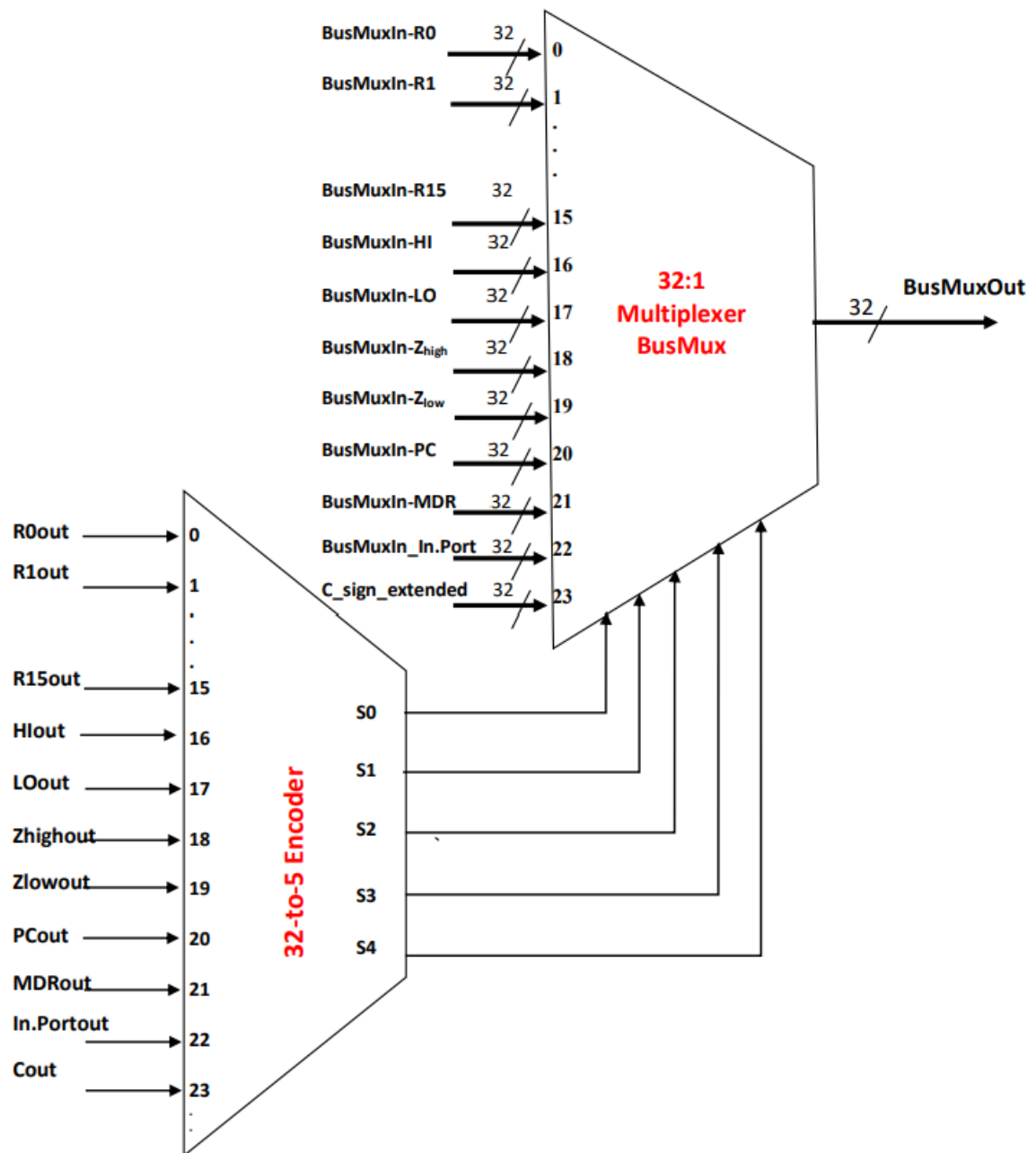


Figure 3: A typical Bus

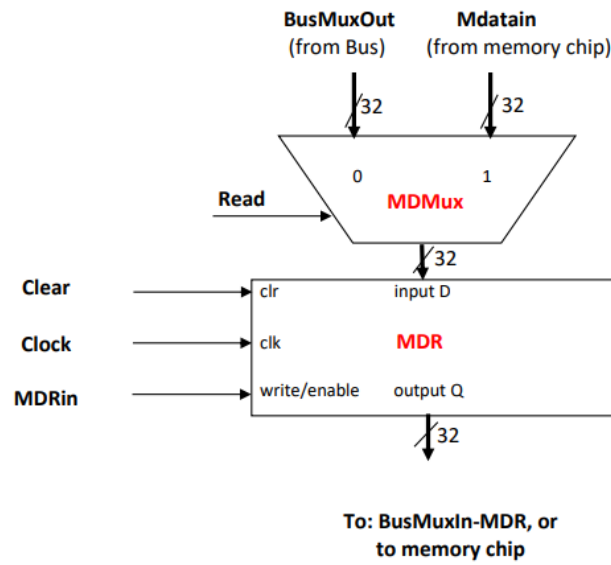


Figure 4: The MDR unit

PHASE 2:

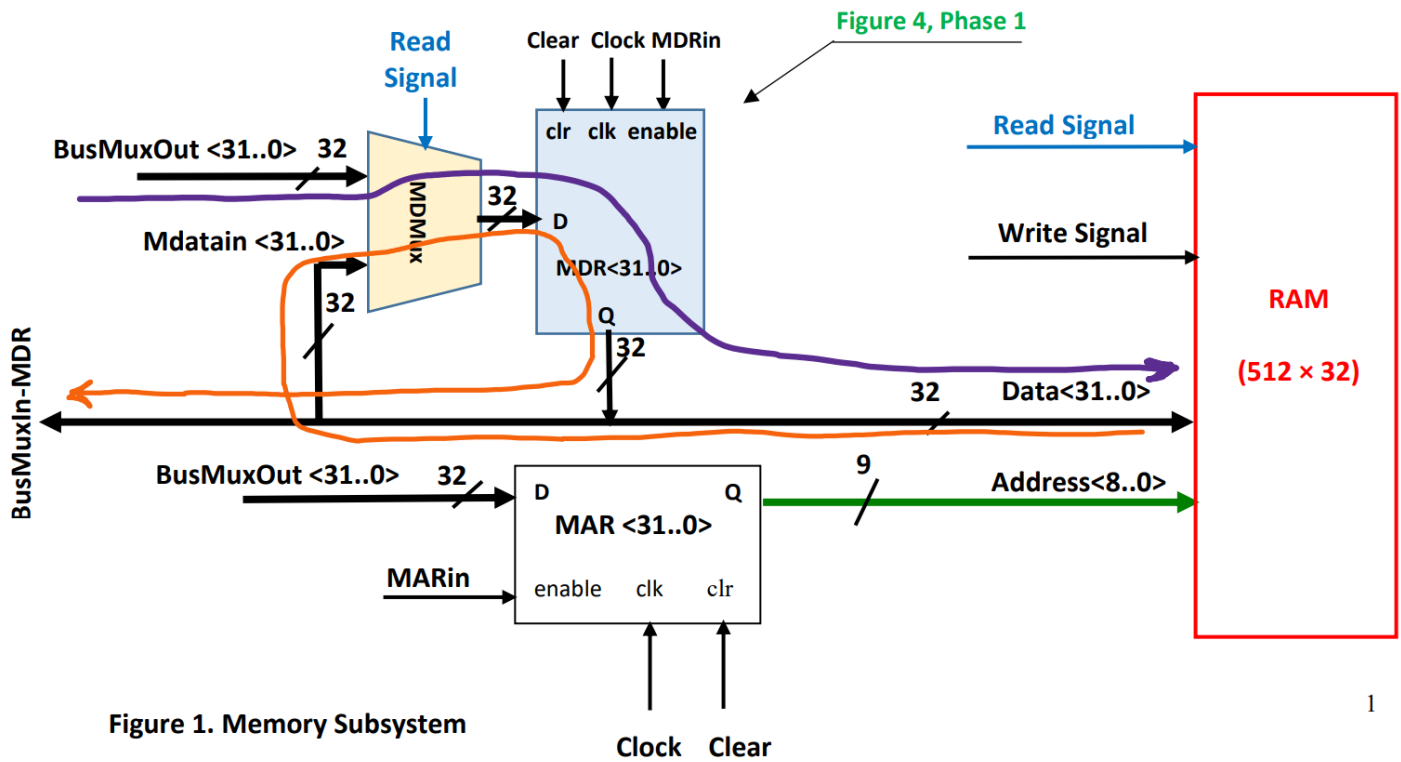


Figure 1. Memory Subsystem

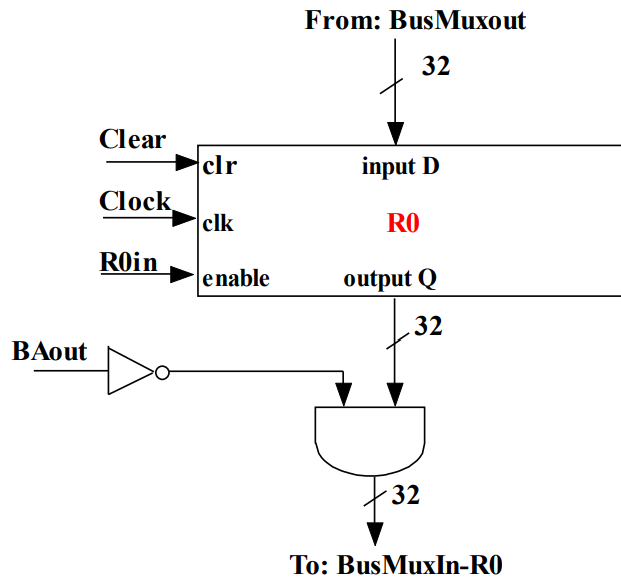


Figure 5. Revised register R0

 


Figure 6. CON FF logic

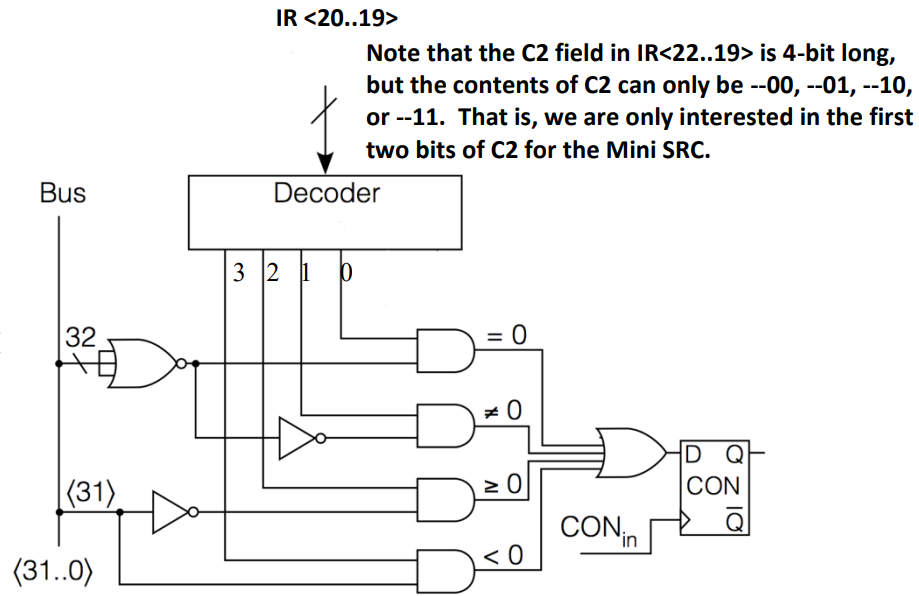


Figure 7. Computation of the conditional value CON in the CON FF Logic

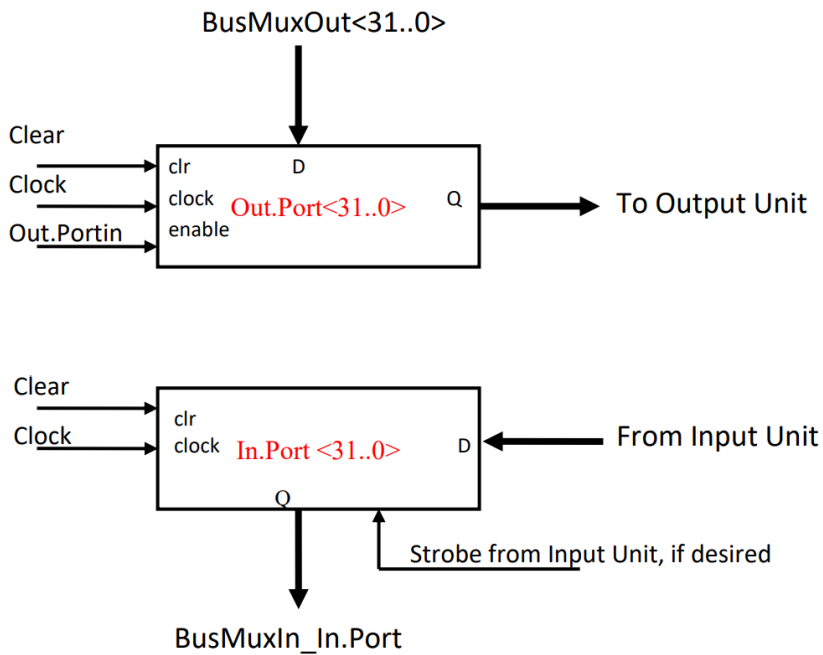


Figure 8. Input and Output ports

PHASE 3:

 


Figure 1: Block diagram of the Control Unit